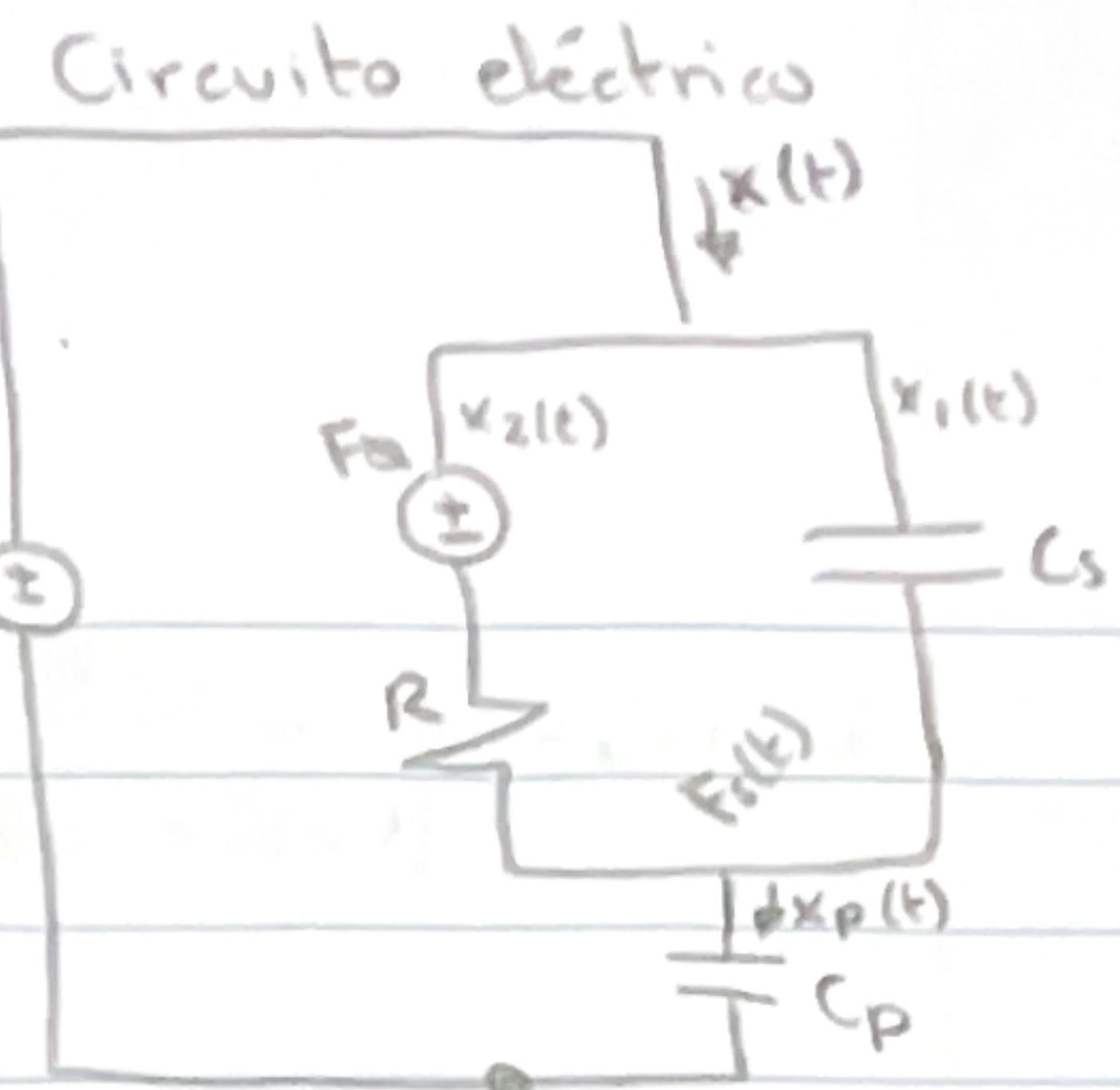


Transformada de Laplace
Derivadas \rightarrow multiplicación por s




Sistema musculosquelético

Función de transferencia

- Análisis por superposición

• Análisis de nodos

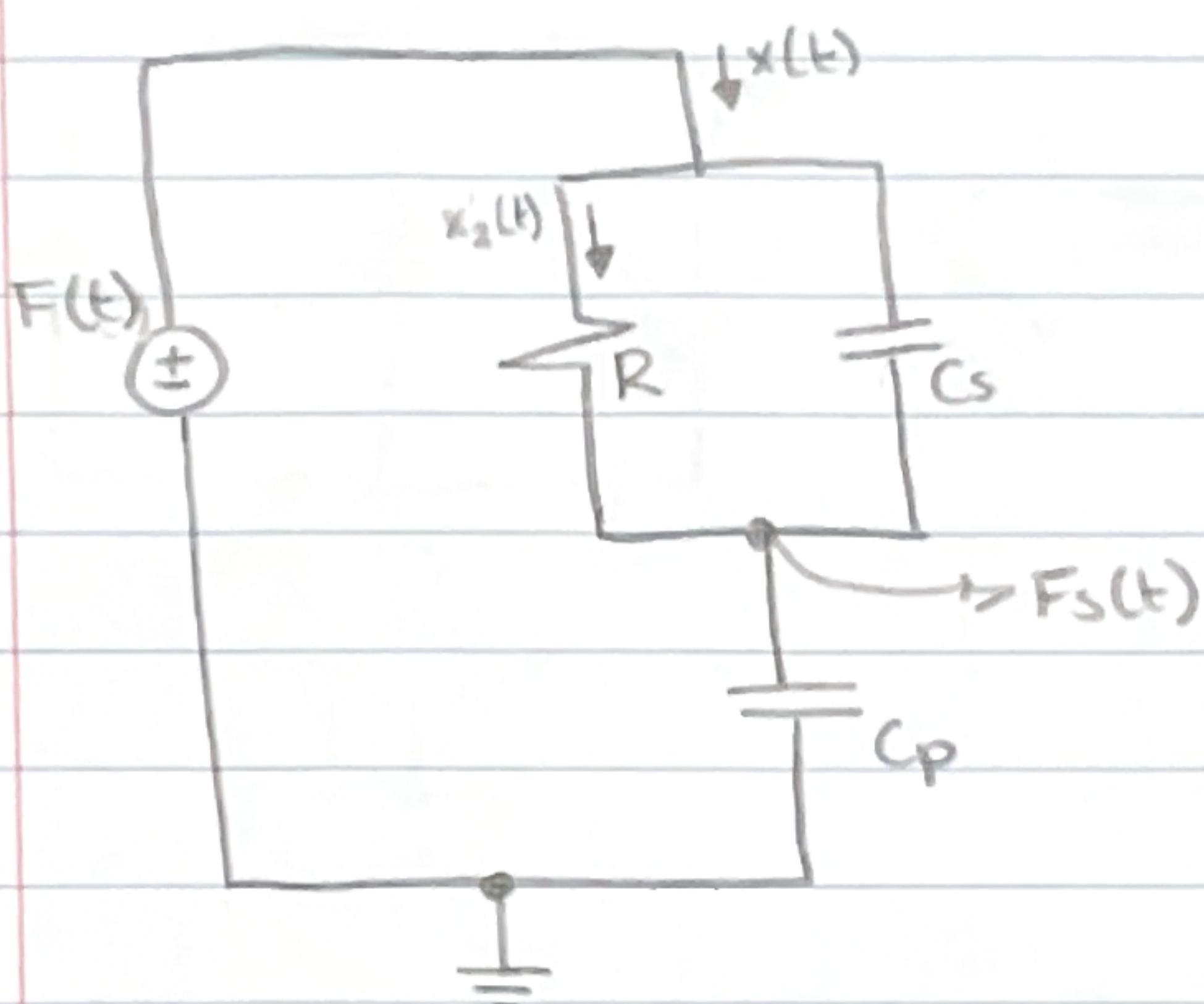

$$x(t) = x_1(t) + x_2(t)$$

$$x(t) = C_p \frac{dF_d(t)}{dt}$$

$$x_1(t) = C_s \frac{d[F(t) - F_d(t)]}{dt}$$

$$x_2(t) = \frac{F(t) - F_d(t)}{R}$$

$$C_p \frac{dF_d(t)}{dt} = C_s \frac{d[F(t) - F_d(t)]}{dt} + \frac{F(t) - F_d(t)}{R}$$

$$\frac{F_d(s)}{F(s)}$$

Transformada de Laplace

$$C_p s F(s) = C_s s [F(s) - F_d(s)] + \frac{F(s) - F_d(s)}{R}$$



$$C_p s F(s) = C_s s F(s) - C_s s F_d(s) + \frac{F(s)}{R} - \frac{F_d(s)}{R}$$

$$(C_p s + C_s s + \frac{1}{R}) F_d(s) = (C_s s + \frac{1}{R}) F(s)$$

$$F_d(s) = \frac{C_s R s + 1}{R} F(s)$$

$$\frac{F_d(s)}{F(s)} = \frac{\frac{C_s R s + 1}{R}}{\frac{C_p R s + C_s R s + 1}{R}} \rightarrow \frac{C_s R + 1}{(C_p R + C_s R)s + 1}$$
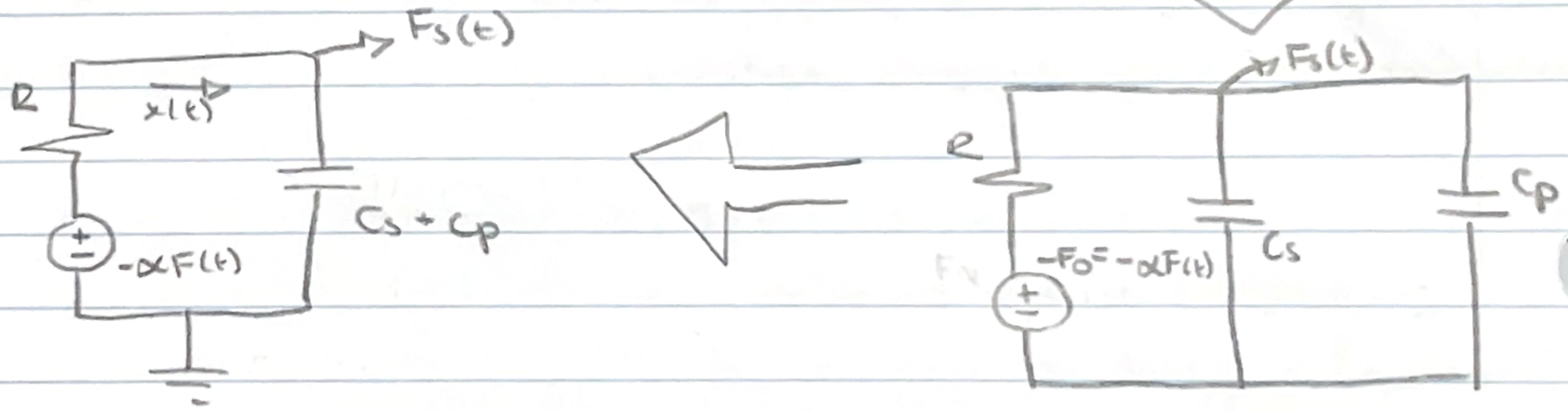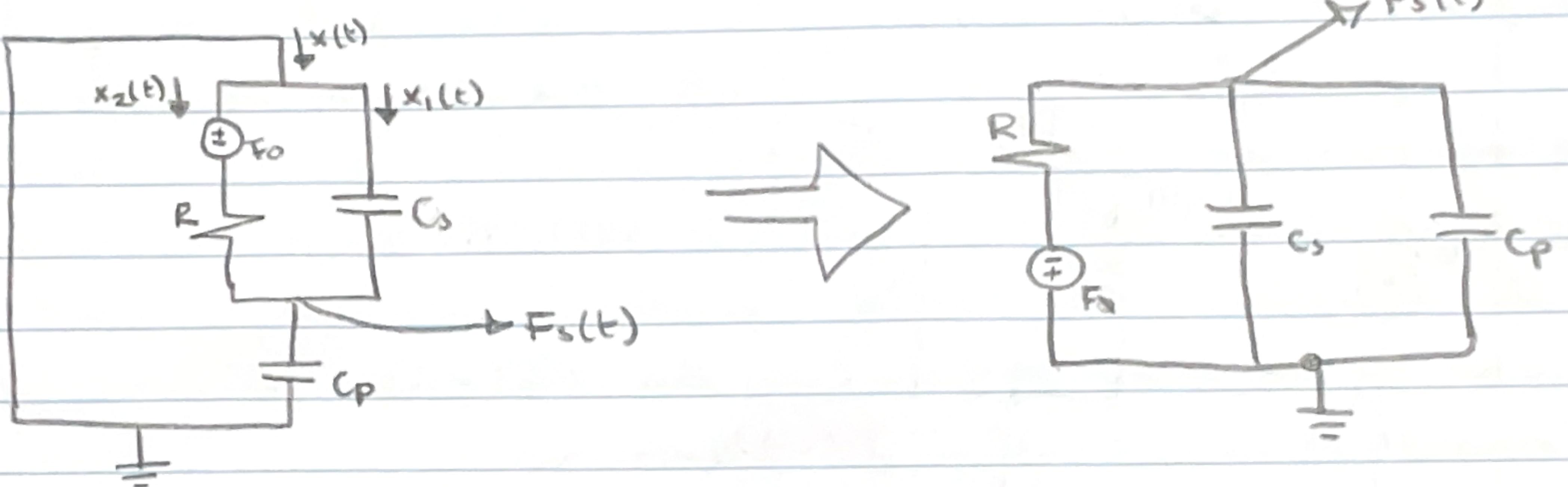
$$F_{S_1}(s) = \frac{C_s R_s + 1}{(C_p R + C_s R)s + 1} F(s)$$



$$-\alpha F(t) = R x(t) + \frac{1}{C_s + C_p} \int x(t) dt$$

$$F_S(t) = \frac{1}{C_s + C_p} \int x(t) dt$$

$$-\alpha F(s) = R x(s) + \frac{x(s)}{(C_s + C_p)s}$$

$$F_S(s) = \frac{x(s)}{(C_s + C_p)s}$$

$$F(s) = \frac{R(C_s + C_p)s + 1}{(C_s + C_p)s} \cdot \frac{x(s)}{-\alpha}$$

$$\frac{F_S(s)}{F(s)} = \frac{\frac{x(s)}{(C_s + C_p)s}}{\frac{R(C_s + C_p)s + 1}{(C_s + C_p)s} \cdot \frac{x(s)}{-\alpha}} \rightarrow \frac{\frac{x(s)}{(C_s + C_p)s}}{\frac{R(C_s + C_p)s + 1}{(C_s + C_p)s} \cdot \frac{x(s)}{-\alpha}}$$

$$\frac{F_s(s)}{F(s)} = \frac{-\alpha}{R(C_s + C_p)s + 1}$$

$$F_{s_2}(s) = \frac{-\alpha F(s)}{R(C_s + C_p)s + 1}$$

$$F(t) = F_{s_1}(s) + F_{s_2}(s)$$

$$F(t) = \frac{(C_s R_s + 1) F(s)}{R(C_s + C_p)s + 1} - \frac{\alpha F(s)}{R(C_s + C_p)s + 1}$$

$$F_s(s) = \frac{C_s R_s + 1 - \alpha}{R(C_p + C_s)s + 1} F(s)$$

Función de transferencia

$$\frac{F_s(s)}{F(s)} = \frac{C_s R_s + 1 - \alpha}{R(C_p + C_s)s + 1} //$$

	Control	Caso
C_s	$10\text{ }\mu\text{F}$	$10\text{ }\mu\text{F}$
C_p	$100\text{ }\mu\text{F}$	$100\text{ }\mu\text{F}$
R	100Ω	$10\text{ k}\Omega$
α	0.25	0.25
$F(t)$	1V	1V


Error en estado estacionario

$$e(s) = \lim_{s \rightarrow 0} s F(s) \left[1 - \frac{F_s(s)}{F(s)} \right]$$

$$e(s) = \lim_{s \rightarrow 0} s * \frac{1}{s} \left[1 - \frac{C_s R_s + 1 - \alpha}{R(C_p + C_s)s + 1} \right]$$

$$e(s) = \alpha$$

$$e(t) = \alpha V$$

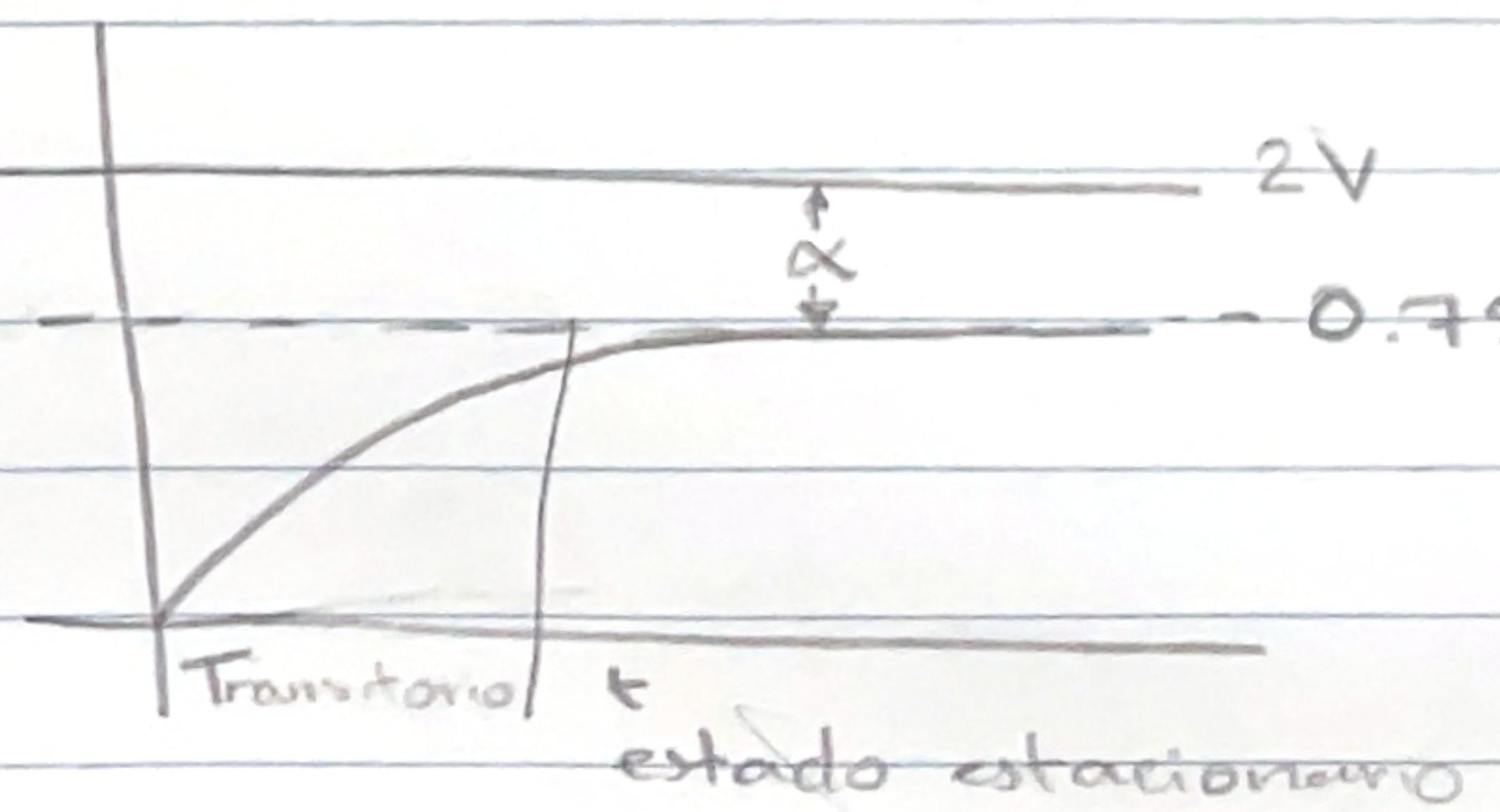

Estabilidad en lazo abierto

$$R(C_p + C_s)s + 1 = \infty$$

$$\lambda = -\frac{1}{R(C_p + C_s)}$$

$\operatorname{Re}\lambda < 0 \rightarrow$ El sistema presenta una respuesta estable